

CR Circuit Response to Step, Pulse, and Square Inputs and Low Pass, High Pass Filter

EE25Btech11063 (Yalamati Vejith),
EE25Btech11064 (Yojit manral)

February 10, 2026

1 Step Input

Step signal is represented as:

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$

Circuit:

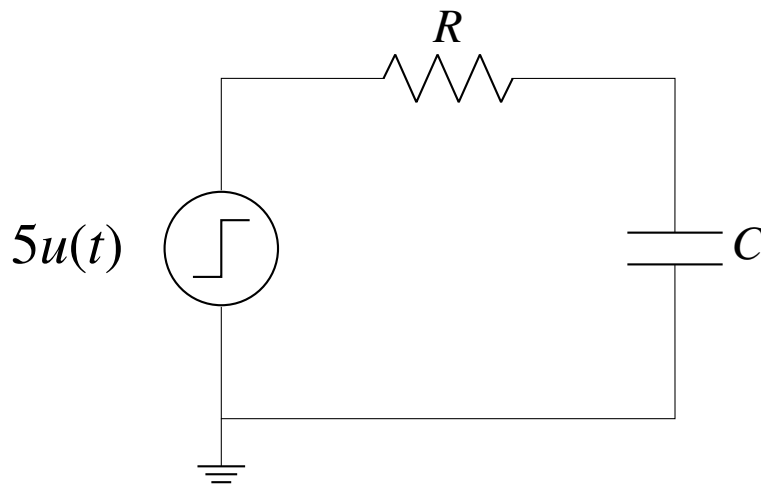


Figure 1: CR Circuit with Step Input

Charging waveform:

According to Kirchhoff's Voltage Law (KVL), the sum of voltages in the loop must equal the input voltage $V_{in}(t)$.

For the charging phase, the input is a step voltage $V_{in}(t) = V \cdot u(t)$

Derivation:

$$V_{in}(t) = V_C(t) + V_R(t) \quad (1)$$

For $t > 0$, $V_{in}(t) = V$.

$$V = \frac{1}{C} \int i(t) dt + i(t)R \quad (2)$$

Differentiating with respect to t :

$$0 = \frac{i(t)}{C} + R \frac{di(t)}{dt} \quad (3)$$

$$\Rightarrow \frac{di}{i} = -\frac{1}{RC} dt \quad (4)$$

$$\int_{I_0}^{i(t)} \frac{1}{i} di = \int_0^t -\frac{1}{RC} dt \quad (5)$$

$$\ln(i) \Big|_{I_0}^{i(t)} = -\frac{t}{RC} \quad (6)$$

$$\ln\left(\frac{i(t)}{I_0}\right) = -\frac{t}{RC} \quad (7)$$

$$\Rightarrow i(t) = I_0 e^{-\frac{t}{RC}} \quad (8)$$

At $t = 0$, the capacitor is uncharged and acts as a short circuit. Thus, $V_R(0) = V$, which means $I_0 = \frac{V}{R}$.

$$i(t) = \frac{V}{R} e^{-\frac{t}{RC}} \quad (9)$$

Since the output is across the resistor, $V_{out}(t) = V_R(t) = i(t)R$:

$$\mathbf{V_{out}(t) = V e^{-\frac{t}{RC}}} \quad (10)$$

Discharging (Step Down)

$$\Rightarrow i(t) = I_0 e^{-\frac{t}{RC}} \quad (11)$$

At $t = 0$, the capacitor acts as a source of voltage V . However, the current now flows out of the capacitor and through the resistor in the opposite direction. Therefore, $V_R(0) = -V$, which means $I_0 = -\frac{V}{R}$.

$$i(t) = -\frac{V}{R} e^{-\frac{t}{RC}} \quad (12)$$

The output voltage is:

$$\mathbf{V_{out}(t) = -V e^{-\frac{t}{RC}}} \quad (13)$$

Conclusion:

Here in the input the value of $V = 5V$ and $R = 820\Omega$ and $C = 1\mu F$

$$\mathbf{V_{out}(t) = \begin{cases} 5e^{-\frac{t}{RC}} \cdot u(t) & \text{for Step-Up (Charging)} \\ -5e^{-\frac{t}{RC}} \cdot u(t) & \text{for Step-Down (Discharging)} \end{cases}} \quad (14)$$

1.1 Waveforms

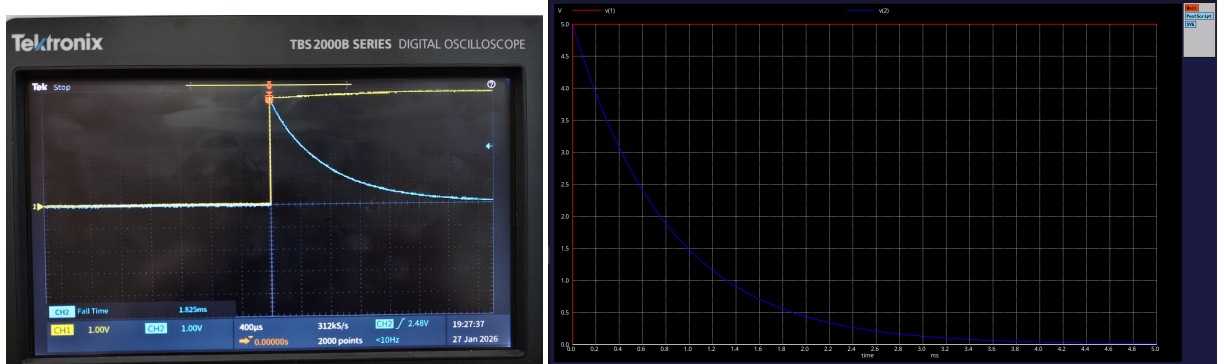


Figure 2: Charging Waveform of CR circuit verified with ngspice simulation

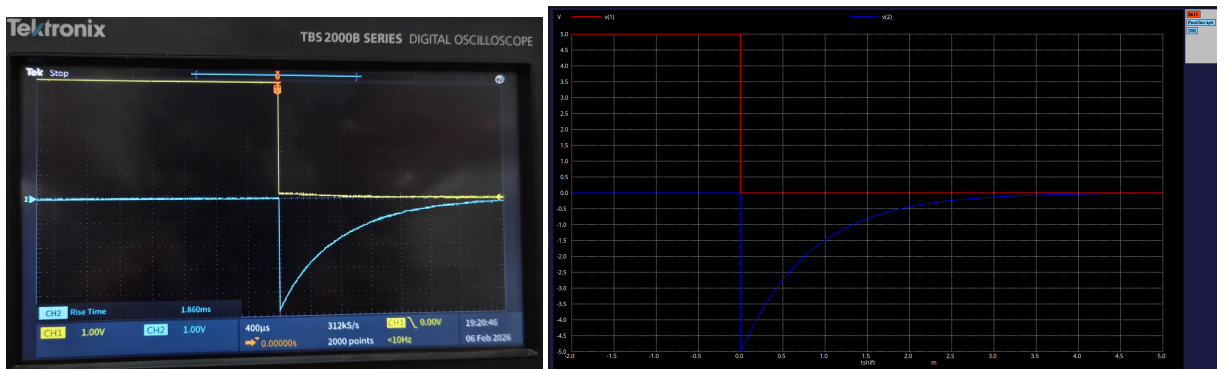


Figure 3: Discharging Waveform of RC circuit verified with ngspice simulation

1.2 Time constant calculation

$$V_R(t) = 5e^{-\frac{t}{RC}} \quad (15)$$

At $t = RC$

$$V_R(t) = 5e^{-1} \quad (16)$$

$$\Rightarrow V_R(t) = 5 \times 0.368 = 1.83V \quad (17)$$

i.e time to taken by the resistor to decrease it's voltage from the peak value to 36.8% of it's peak voltage is defined as Time constant(τ) of the circuit.

From the waveforms obtained in DSO we get the time constant as

$$\tau \approx 820\mu s \quad (18)$$

Fall Time:

The rise time (t_r) of an CR circuit is defined as the time required for the output pulse to decay from 90% of its peak value down to 10% of its peak value.

$$\Rightarrow \tau = \frac{t_r}{2.2} \quad (19)$$

$$\Rightarrow \tau = \frac{1825}{2.2} \mu s \quad (20)$$

$$\tau \approx 830 \mu s \quad (21)$$

Error:

$$\text{Error} = \frac{830 - 820}{820} \times 100\% \quad (22)$$

$$\Rightarrow = \frac{10}{820} \times 100\% \quad (23)$$

$$\Rightarrow \text{Error} \approx 1.22\% \quad (24)$$

Experimental value of time constant almost matches the original value of time constant with an error $<1.5\%$

Conclusion:

- In the case of a charging waveform for step input for $t > 0$ the voltage across the resistor will exponentially decrease to the relation $V_R(t) = 5e^{-\frac{t}{RC}}$
- In the case of a discharging waveform for a step input the voltage across the resistor will exponentially increase from -5V to 0V according to the relation $V_R(t) = -5e^{-\frac{t}{RC}}$
- The above results match exactly with the ngspice simulations.

2 Pulse input

Pulse input is given by:

$$x(t) = \begin{cases} 0, & t < 0 \\ 5, & 0 \leq t < T \\ 0, & t \geq T \end{cases}$$

Circuit:

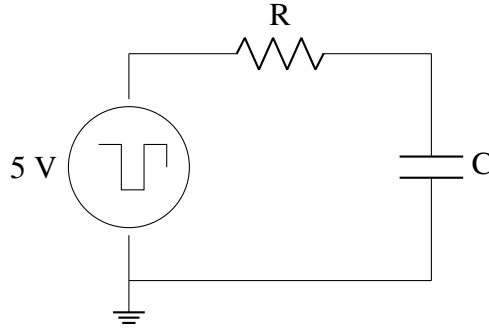


Figure 4: CR Circuit with Pulse Input

Explanation:

- From $t = 0$ to t_{on} voltage of the resistor will decay according to the relation $V_R(t) = 5e^{-\frac{t}{RC}}$
- When the input V_{in} transitions abruptly from 5V to 0V at $t = t_{on}$:

$$V_R(T_{on}) = V_{in}(T_{on}) - V_C(T_{on}^-) \quad (25)$$

$$V_R(T_{on}) = 0 - V_C \implies V_R = -V_C \quad (26)$$

- This creates a sharp jump into the negative region of the oscilloscope display.
- During the interval where $V_{in} = 0$, the capacitor discharges through the resistor. The discharge current $I(t)$ flows in the opposite direction to the charging current. The voltage of the resistor is governed by:

$$V_R(t) = -5 \cdot e^{-\frac{t}{RC}} \quad (27)$$

- As the time increases where $V_{in} = 0$ the voltage of the resistor tends to 0 according to (27)

2.1 Wave forms

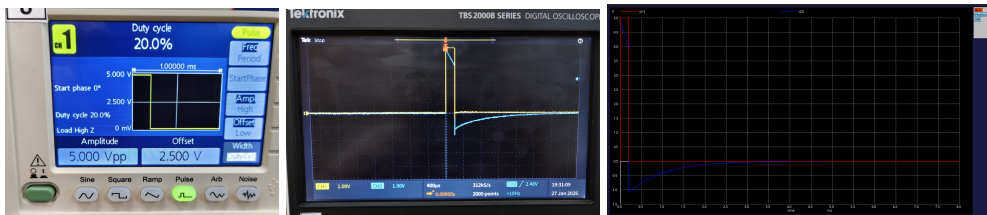


Figure 5: CR Circuit with Pulse of with 20% duty cycle

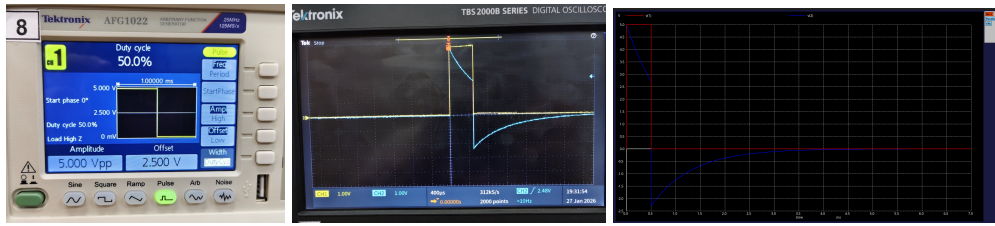


Figure 6: CR Circuit with Pulse Input of 50% duty cycle

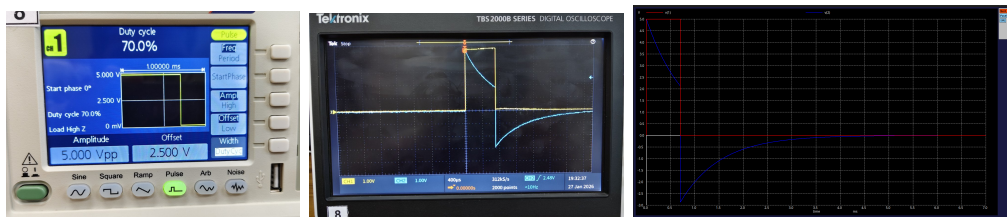


Figure 7: CR Circuit with Pulse Input of 70% duty cycle

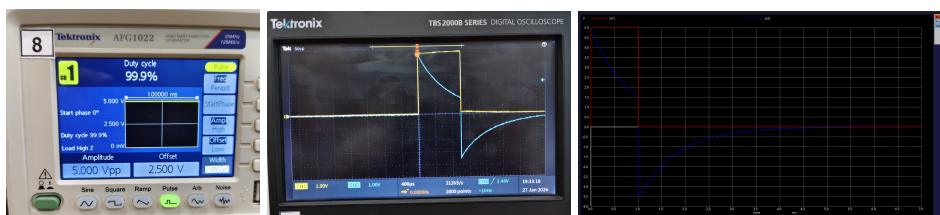


Figure 8: CR Circuit with Pulse Input of 99.9% duty cycle

Comparison Table:

Let t' be the on time i.e the time where the voltage transition occurs from 5V to 0V

Duty Cycle(%)	$V_R(t'-)$	$V_R(t'+)$
20.0	3.916V	-1.1V
50.0	2.72V	-2.28V
70.0	2.13V	-2.87V
99.9	1.48V	-3.52V

Conclusion:

- As the duty cycle the voltage of the resistor at the transition time decreases
- After that the voltage of resistor starts from $-V_C(t)$ and gradually attains 0V as time progress

3 Square-Wave input

The square wave input voltage $v_{in}(t)$ with a period T is defined as:

$$v_{in}(t) = \begin{cases} 5, & 0 \leq t < \frac{T}{2} \\ 0, & \frac{T}{2} \leq t < T \end{cases} \quad (28)$$

with the periodicity condition $v_{in}(t + T) = v_{in}(t)$.

Circuit:

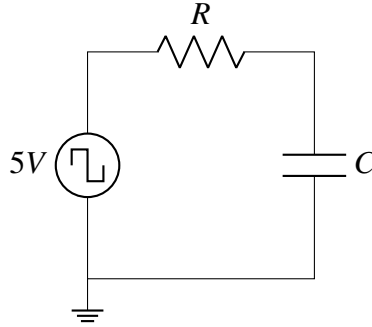


Figure 9: CR Circuit with a 5V Square Wave Input

3.1 $CR \gg T$

In this case the value of $\tau = 820\mu s$ so, let's take the frequency of the square wave as 100kHz. Then, $T = 10\mu s$

Calculation:

- $V_R(t) = 5 \cdot e^{-\frac{t}{RC}} \implies V_R(t) = V_{in}(t) - V_C(t)$
- Capacitor takes ≈ 5 time constants to charge. i.e $\approx 4.1ms$.
- The pulse width is very short ($5\mu s$). This is less than 1% of the time constant. During the "ON" cycle, the capacitor has time to begin charging before the input switches "OFF".
- The capacitor cannot follow the rapid switching of the input. It settles at the point where the charge accumulating during the "ON" phase $\approx$ equals the charge draining during the "OFF" phase.
- In the **Steady State**, the capacitor reaches an average charge equal to the DC component of the input. For a 0V to 5V square wave, the average value is 2.5V.
- At $t(0^+)$, the input jumps from 0V to 5V. Since $V_C \approx 2.5V$, the output is:

$$V_R(0^+) = V_{in}(0^+) - V_C \approx 5V - 2.5V = 2.5V \quad (29)$$

- Similarly, when the input drops to 0V:

$$V_R(t_{fall}^+) = 0V - 2.5V = -2.5V \quad (30)$$

- The exponential decay seen at 1 kHz is now nearly invisible. So, it is difficult to capture transient response in this case. The steady state looks like a flat-top square wave centered at 0V.

Waveforms

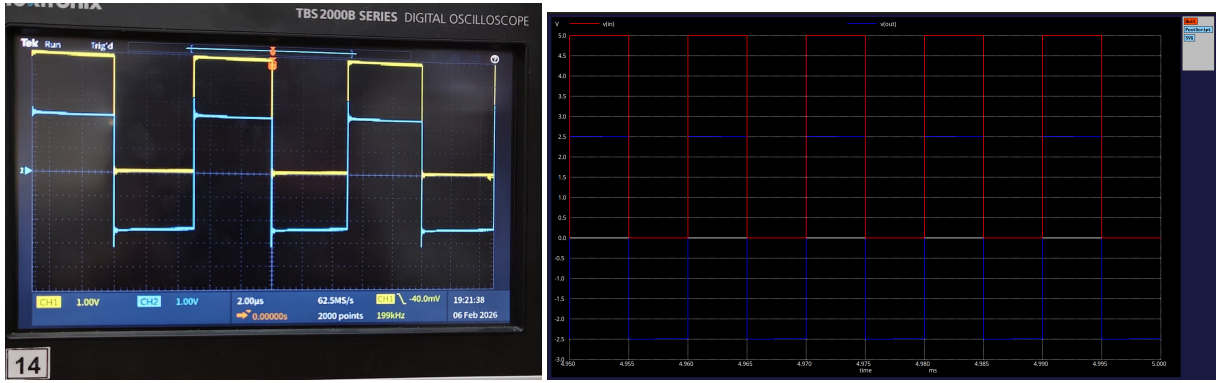


Figure 10: CR>>T case verified with ngspice simulation

3.2 RC ≈ T

The value of $\tau = 820\mu s$ so, let's take the frequency of the square wave as 1kHz. Then, $T = 1000\mu s$.

For a square wave of time period T it's value is 5v for $\frac{T}{2}$ and 0 for remaining time.

Calculation:

- At $t = 0$, the capacitor is uncharged ($V_C(0^-) = 0V$). Because V_C cannot change instantaneously:

$$V_R(0^+) = V_{in}(0^+) - V_C(0^-) = 5V - 0V = 5V \quad (31)$$

- As t approaches 0.5 ms,

$$V_R(t) = e^{-\frac{500}{820}} \quad (32)$$

$$\implies V_R(t) = 2.72V \text{ and } V_C(t) = 2.28V \quad (33)$$

- When the input drops to 0V, the resistor voltage becomes:

$$V_R(0.5 \text{ ms}^+) = 0V - 2.28V = -2.28V \quad (34)$$

- from $t = 0.5\text{ms}$ to $t = 1\text{ms}$ $V_R(t) = 0 - V_C(t)$

$$V_R(t) = -2.28 \cdot e^{-\left(\frac{t-0.5}{RC}\right)} \quad (35)$$

$$\Rightarrow V_C(1\text{ ms}^-) = 2.28 \times e^{-0.61} \quad (36)$$

$$\Rightarrow V_C(1\text{ ms}^-) = 1.24\text{V} \quad (37)$$

- when $t > 1\text{ms}$ $V_C(1\text{ ms}^+) = V_C(1\text{ ms}^-) = 1.24\text{V}$

$$V_R(t) = 3.76\text{V} \quad (38)$$

- At final, in steady state the output settles at $\pm 3.24\text{V}$.

Waveforms

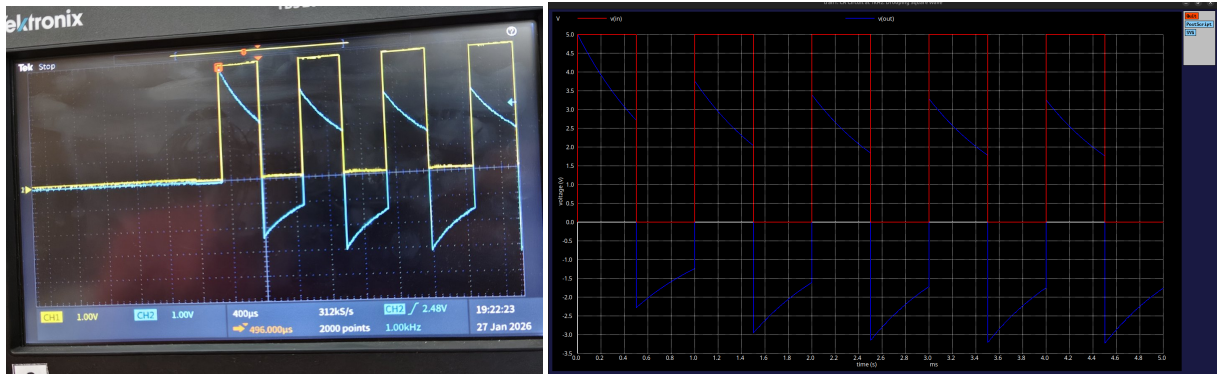


Figure 11: $CR \approx T$ case Transient response verified with ngspice simulation

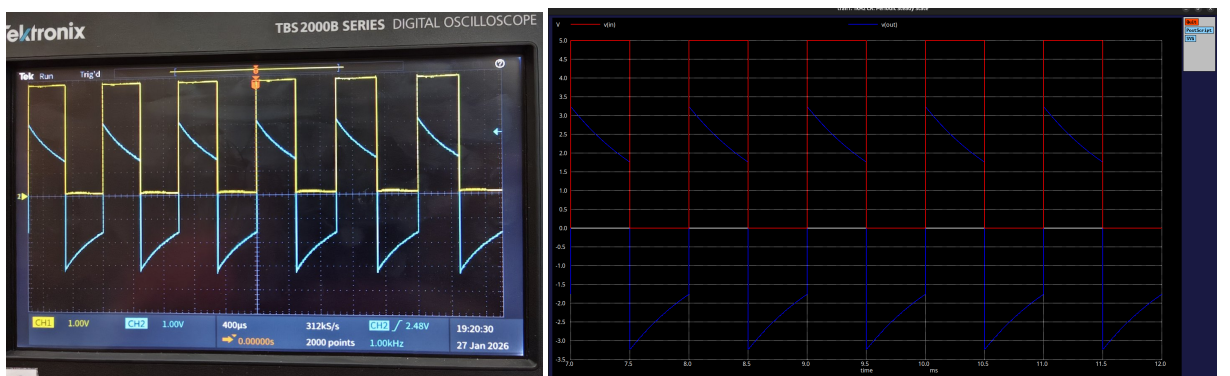


Figure 12: $CR \approx T$ case Steady state verified with ngspice simulation

3.3 $RC \ll T$

In this case the value of $\tau = 820\mu s$ so, let's take the frequency of the square wave as 1Hz. Then, $T = 1s$.

Calculation:

- Capacitor takes $\approx 5\tau$ to charge completely so it takes around 4.1ms to charge completely but the on time of the square wave is very high i.e 0.5s.
- So Capacitor takes $<1\%$ of the on time completely so most of the time capacitor acts as open circuit. so, $V_R(t) = V_{in} - V_C(t) = 0$ when capacitor acts as open circuit.
- When the input square wave is at a steady 5V or 0V, the capacitor acts as an open circuit ($I = 0$). By Ohm's Law, $V_R = IR = 0V$. This results in the long horizontal segments observed on the 0V axis in the DSO and simulation traces.
- The voltage of the resistor is proportional to current through it.

$$V_R(t) = R \cdot i(t) \quad (39)$$

$$\Rightarrow V_R(t) = RC \frac{dV_C}{dt} \quad (40)$$

$$V_R(t) \approx RC \frac{dV_{in}}{dt} \quad (41)$$

At the transition edges of a square wave, the derivative $\frac{dV_{in}}{dt}$ is a Dirac delta-like pulse.

- Generally the dirac delta function is represented as

$$\delta(t) = \begin{cases} +\infty, & t = 0 \\ 0, & t \neq 0 \end{cases} \quad (42)$$

- The rising edge produces a positive impulse $+\delta(t)$, while the falling edge produces a negative impulse $-\delta(t)$, explaining the alternating upward and downward "needles" seen in the steady-state graph.

Wave forms:

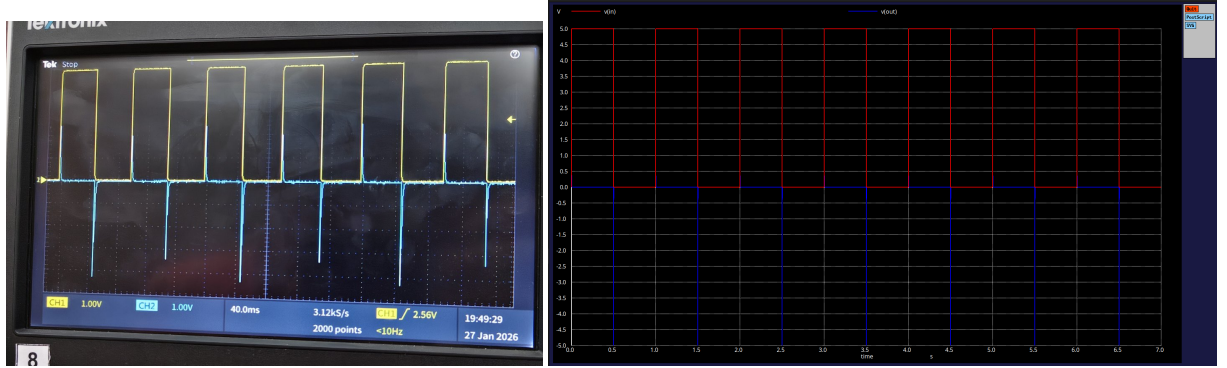


Figure 13: $CR \ll T$ case Steady state verified with ngspice simulation

4 Low Pass Filter

- **Definition:** A low pass filter circuit is a filter that passes signals with frequencies lower than cutoff frequency (f_c) while attenuating (reducing the amplitude of) signals with frequencies higher than that cutoff.
- **Cut-off frequency:** The point where the output signal amplitude falls to 70.7% (-3 dB) of the input signal voltage.
- In a standard RC Low-Pass Filter, the output voltage (V_{out}) is measured across the capacitor.

4.1 Calculations

Gain:

- $\text{gain} = \frac{|V_{out}|}{|V_{in}|}$
- The impedances of the resistor and capacitor are $Z_R = R$ and $Z_C = \frac{1}{j\omega C}$, respectively. The transfer function is given by:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} \quad (43)$$

Substituting the impedance values:

$$H(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} \quad (44)$$

$$\Rightarrow \text{gain} = |H(\omega)| = \sqrt{H(\omega) \cdot H^*(\omega)} = \frac{1}{\sqrt{1^2 + (\omega RC)^2}} \quad (45)$$

- The cut-off frequency is defined as the point where the gain magnitude is $1/\sqrt{2}$ of the maximum gain. Setting the equation (45) equal to this value:

$$\frac{1}{\sqrt{1 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}} \quad (46)$$

Squaring both sides and solving for ω_c :

$$1 + (\omega_c RC)^2 = 2 \implies (\omega_c RC)^2 = 1 \implies \omega_c = \frac{1}{RC} \quad (47)$$

$$2\pi f_c = \frac{1}{RC} \implies f_c = \frac{1}{2\pi RC} \quad (48)$$

- Equation 45 can be written using cutoff frequency as $\omega_c = \frac{1}{RC}$,

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}} \quad (49)$$

4.2 Bode plots

Magnitude response (dB) vs frequency on log scale :

- **Y-axis:** The values on the y-axis are represented by the power gain in decibels, calculated as:

$$Y_{dB} = 20 \cdot \log_{10}(\text{Gain}) \quad (50)$$

- **X-axis:** While the actual frequency values (f) are labeled on the x-axis, the physical distance between them is measured on a **logarithmic scale**.
- **Scale Characteristic:** This means that the distance between any two decades is constant. For example, the physical distance between 10^2 Hz and 10^3 Hz is exactly the same as the distance between 10^3 Hz and 10^4 Hz.

Phase response vs frequency on log scale :

- **Y-axis:** The values on the y-axis are the phase difference between the waves of output and input measured in degrees.
- **X-axis:** While the actual frequency values (f) are labeled on the x-axis, the physical distance between them is measured on a **logarithmic scale**.
- From (44) The phase shift ϕ introduced by the filter is the argument of the transfer function:

$$\phi(\omega) = \angle H(\omega) = -\tan^{-1}(\omega RC) = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right) \quad (51)$$

- when $\omega \ll \omega_c$ phase difference between them is nearly 0° . At the cutoff frequency ($\omega = \omega_c$), the phase shift is -45° . At $\omega \gg \omega_c$ phase difference between them is $\approx -90^\circ$.

Note:

- In DSO we measured phase difference with respect to ch1 i.e ch1 - ch2 is the measured value on DSO. But, the required one is ch2 - ch1. So negative of phase difference observed is plotted
- Mathematically according to the calculations the minimum phase difference is $\approx -90^\circ$. But, actually in DSO when $\omega \gg \omega_c$ the output is almost not detected and the phase difference observed in the DSO will be $< -90^\circ$
- So, in DSO if phase difference $< -90^\circ$ the phase difference can be taken as $\approx -90^\circ$

4.3 Wave forms

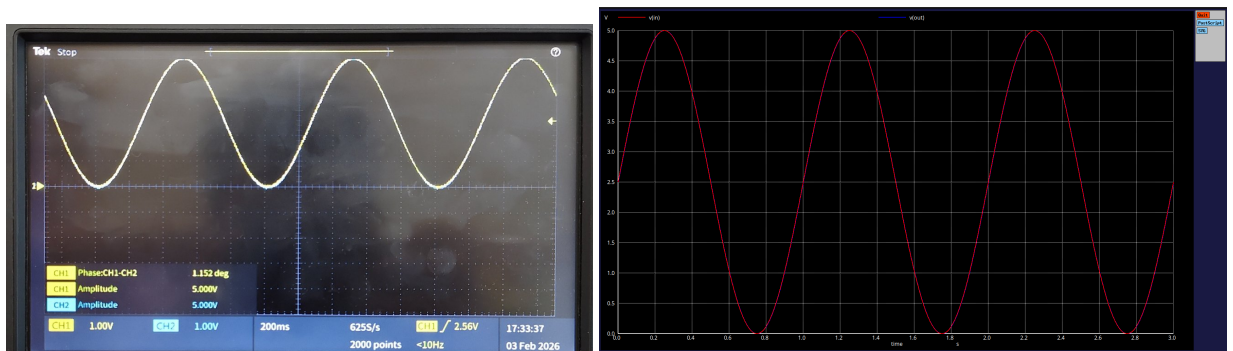


Figure 14: Low pass filter with frequency 1Hz

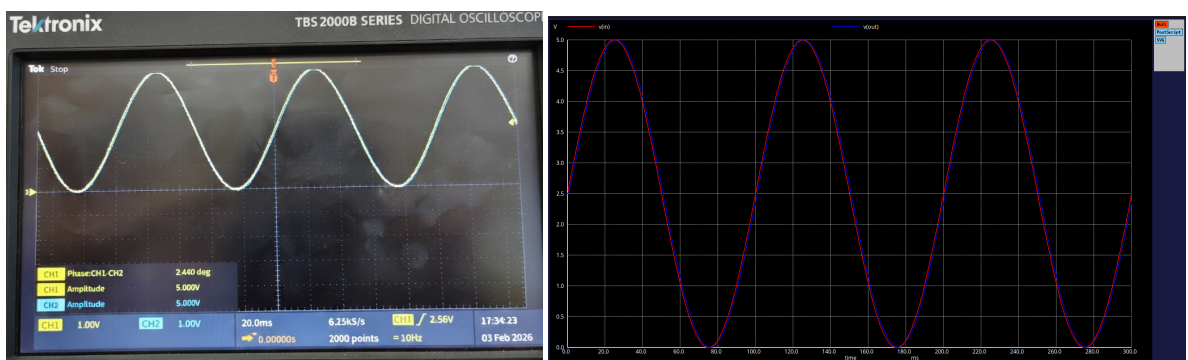


Figure 15: Low pass filter with frequency 10Hz

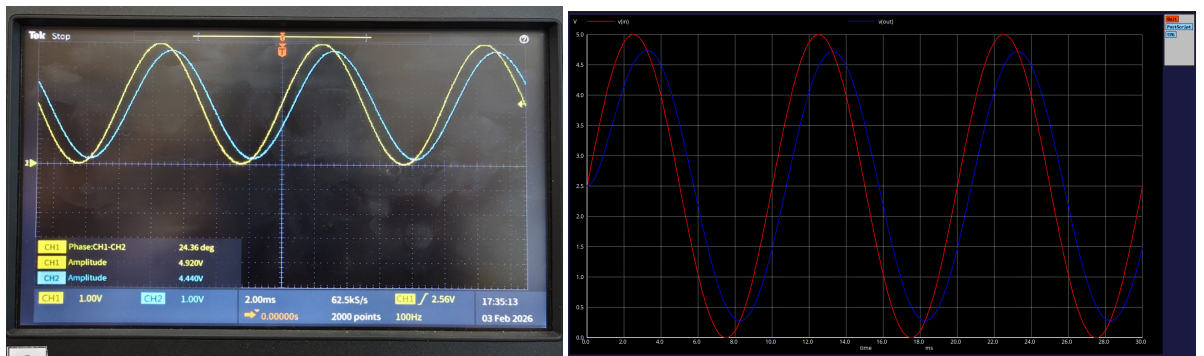


Figure 16: Low pass filter with frequency 100Hz

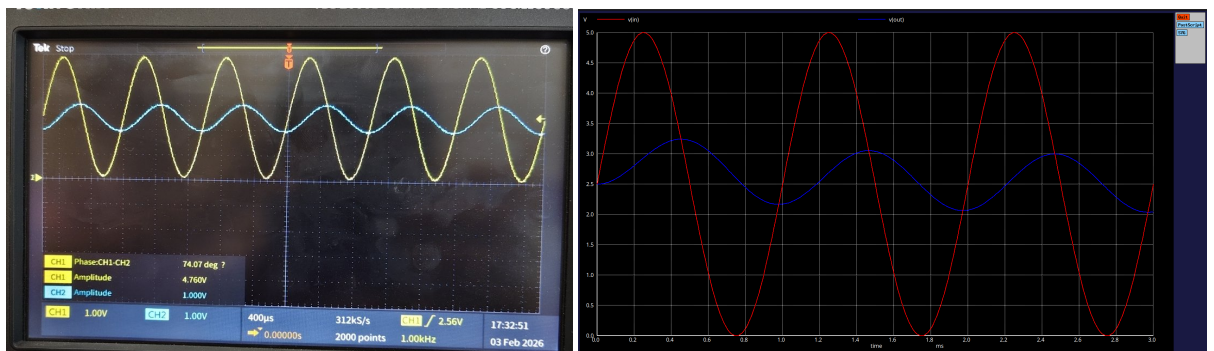


Figure 17: Low pass filter with frequency 1KHz

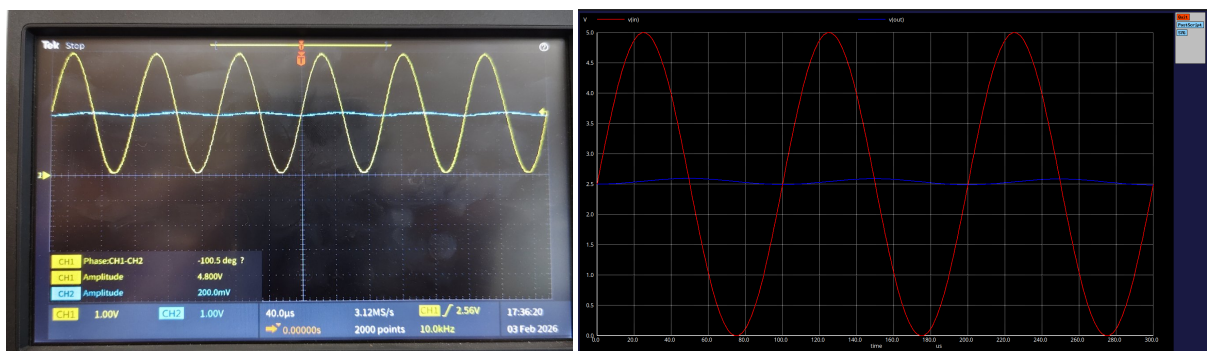


Figure 18: Low pass filter with frequency 10KHz

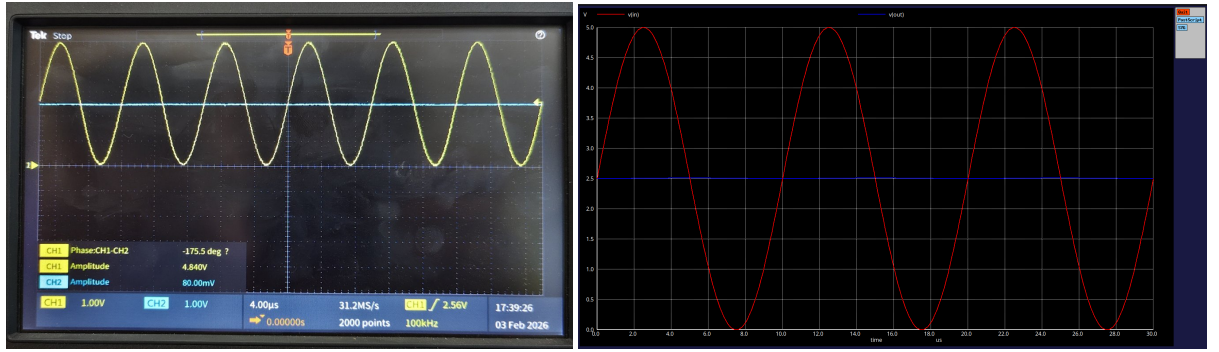


Figure 19: Low pass filter with frequency 100KHz

Cut-off frequency:

Cut-off frequency for the given circuit ($R = 820\Omega$ and $C = 1\mu F$) given by

$$f_c = \frac{1}{2\pi RC} \quad (52)$$

$$\Rightarrow f_c = \frac{1}{2\pi \times 820 \times 10^3 \times 1 \times 10^{-6}} \quad (53)$$

$$\Rightarrow f_c = 194.09 \text{ Hz} \quad (54)$$

Frequency (Hz)	Linear Gain $ H(f) $	Output Voltage V_{out} (V)	Gain (dB)
1	0.9999	5.000	-0.0001
10	0.9987	4.993	-0.0115
100	0.8889	4.445	-1.0225
10^3	0.1905	0.953	-14.4005
10^4	0.0194	0.097	-34.2415
10^5	0.0019	0.010	-54.2399

Table 1: Gain at different frequencies ($R = 820\Omega$, $C = 1\mu F$, $V_{in} = 5V$)

The above Theoretical values almost matches the experimental data

Note:

The experimental input amplitude measured was $< 5.0V$ in some cases. This error can be attributed to the following factors:

- The 50Ω internal source impedance of the function generator creates a voltage divider with the circuit's input impedance, slightly reducing the voltage delivered to the nodes.
- The DSO vertical resolution at $1V/\text{div}$ may introduce a small measurement offset during the analog-to-digital conversion process.

4.4 Graphs:

Magnitude Response

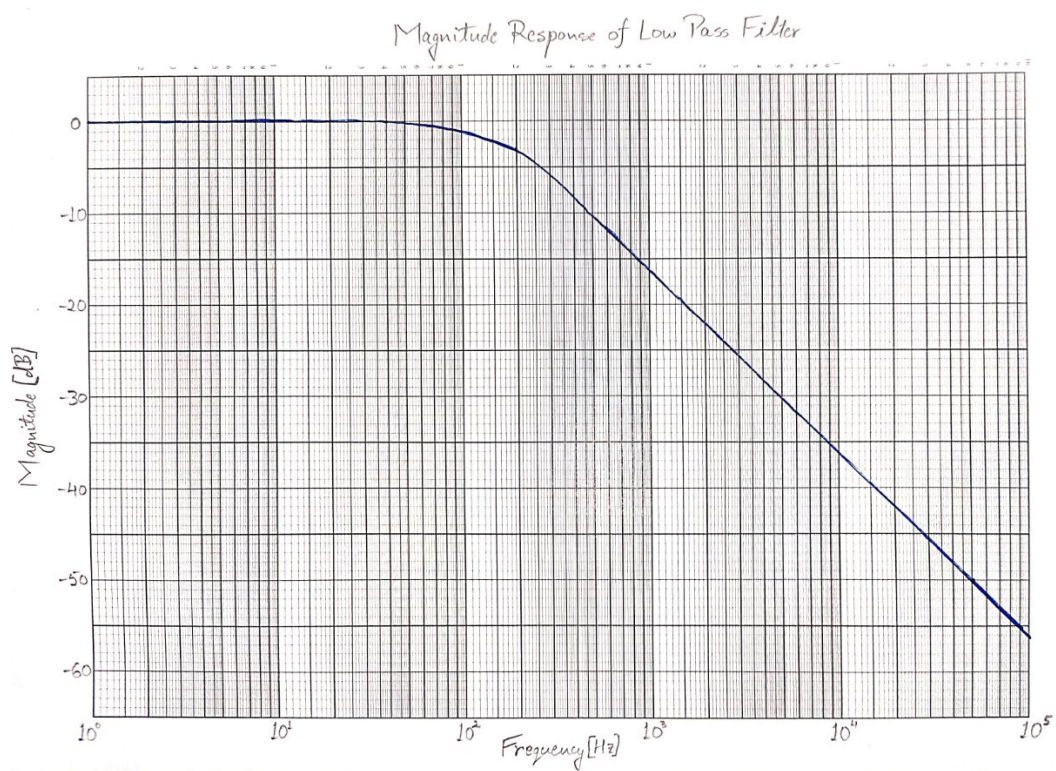


Figure 20: Experimental Plot of a High pass filter

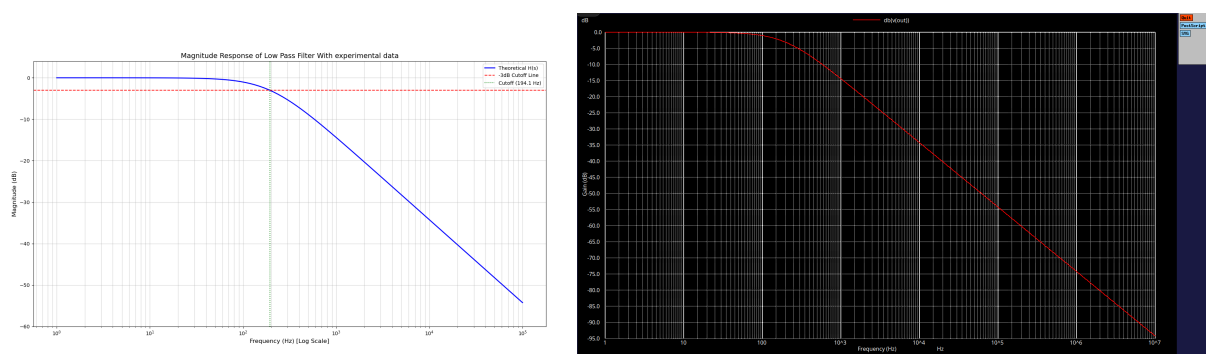


Figure 21: Python plot and ngspice plot of a Low pass filter

Experimental graph plotted matches exactly with the python plot and ngspice plot

Phase Response

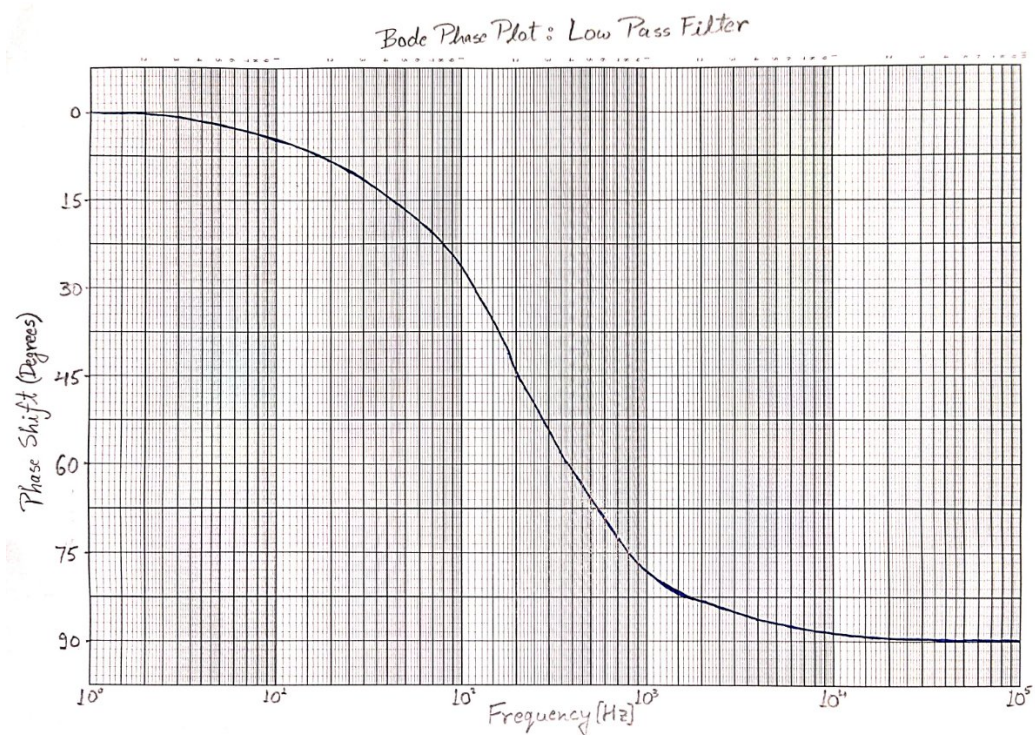


Figure 22: Experimental Plot of a Low pass filter

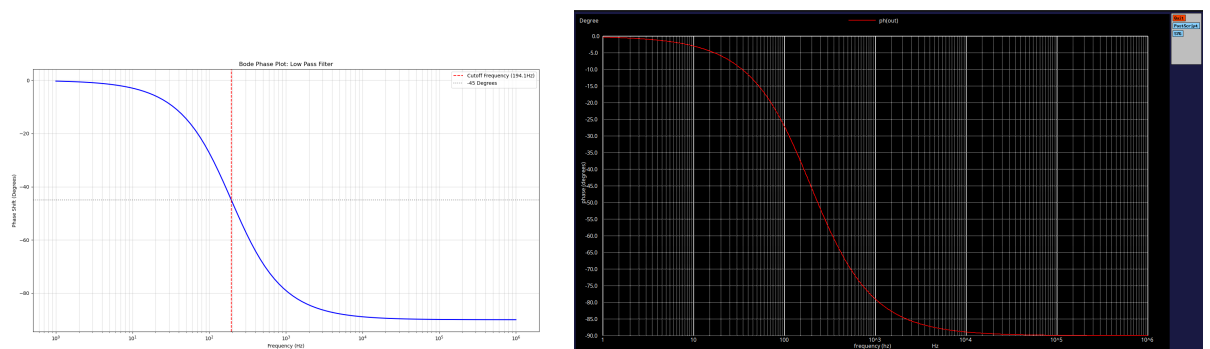


Figure 23: Python plot and ngspice plot of a Low pass filter

Above Experimental graph of phase response of Low pass filter matches exactly with the python plot and ngspice plot

Slope

- $\omega < \omega_c$, the slope is approximately 0 dB/decade. Means the signal passes through with almost no loss in amplitude.

- $\omega = \omega_c$ This is the point of the curve where the slope begins to transition.
- $\omega > \omega_c$ The slope becomes a constant -20 dB/decade.

5 High Pass Filter

- **Definition:** A High pass filter circuit is a filter that passes signals with frequencies higher than cutoff frequency (f_c) while attenuating (reducing the amplitude of) signals with frequencies lower than that cutoff.
- **Cut-off frequency:** The point where the output signal amplitude falls to 70.7% (-3 dB) of the input signal voltage.
- In a standard RC High-Pass Filter, the output voltage (V_{out}) is measured across the resistor.

5.1 Calculations

Gain:

- gain = $\frac{|V_{out}|}{|V_{in}|}$
- The impedances of the resistor and capacitor are $Z_R = R$ and $Z_C = \frac{1}{j\omega C}$, respectively. For a high-pass filter, the output is taken across the resistor. The transfer function is given by:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_R}{Z_R + Z_C} \quad (55)$$

Substituting the impedance values:

$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} \quad (56)$$

$$\Rightarrow \text{gain} = |H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \quad (57)$$

- The cut-off frequency is defined as the point where the gain magnitude is $1/\sqrt{2}$ of the maximum gain. Setting equation (57) equal to this value:

$$\frac{\omega_c RC}{\sqrt{1 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}} \quad (58)$$

Squaring both sides and solving for ω_c :

$$\frac{(\omega_c RC)^2}{1 + (\omega_c RC)^2} = \frac{1}{2} \implies (\omega_c RC)^2 = 1 \implies \omega_c = \frac{1}{RC} \quad (59)$$

$$2\pi f_c = \frac{1}{RC} \implies f_c = \frac{1}{2\pi RC} \quad (60)$$

- Equation 57 can be written using cutoff frequency as $\omega_c = \frac{1}{RC}$. Dividing numerator and denominator by ωRC :

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}} \quad (61)$$

5.2 Bode Plots

Magnitude response (dB) vs frequency on log scale :

- **Y-axis:** The values on the y-axis are represented by the power gain in decibels, calculated as:

$$Y_{dB} = 20 \cdot \log_{10}(\text{Gain}) \quad (62)$$

- **X-axis:** While the actual frequency values (f) are labeled on the x-axis, the physical distance between them is measured on a **logarithmic scale**.
- **Scale Characteristic:** This means that the distance between any two decades is constant. For example, the physical distance between 10^2 Hz and 10^3 Hz is exactly the same as the distance between 10^3 Hz and 10^4 Hz.

Phase response vs frequency on log scale :

- **Y-axis:** The values on the y-axis are the phase difference between the waves of output and input measured in degrees.
- **X-axis:** While the actual frequency values (f) are labeled on the x-axis, the physical distance between them is measured on a **logarithmic scale**.
- From (56) The phase shift ϕ introduced by the filter is the argument of the transfer function:

$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC} \quad (63)$$

$$\phi(\omega) = \angle H(\omega) = \frac{\pi}{2} - \tan^{-1}(\omega RC) = \tan^{-1}\left(\frac{1}{\omega RC}\right) = \tan^{-1}\left(\frac{\omega_c}{\omega}\right) \quad (64)$$

- when $\omega \ll \omega_c$ phase difference between them is $\approx 90^\circ$. At the cutoff frequency ($\omega = \omega_c$), the phase shift is 45° . At $\omega \gg \omega_c$ phase difference between them is $\approx 0^\circ$.

Note:

- In DSO we measured phase difference with respect to ch1 i.e ch1 - ch2 is the measured value on DSO. But, the required one is ch2 - ch1. So negative of phase difference observed is plotted
- Mathematically according to the calculations the maximum phase difference is $\approx 90^\circ$. But, actually in DSO when $\omega \ll \omega_c$ the output is almost not detected and the phase difference will go beyond 90°
- So, in DSO if phase difference $> 90^\circ$ the phase difference can be taken as $\approx 90^\circ$

5.3 Waveforms

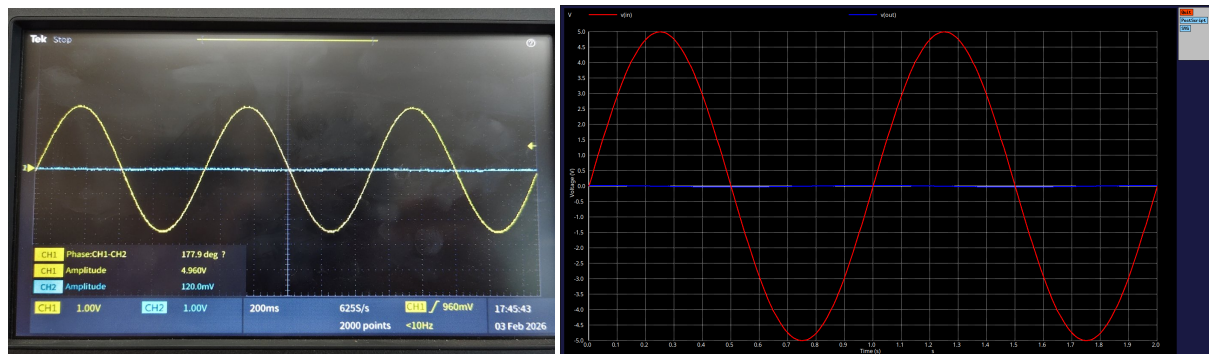


Figure 24: High pass filter with frequency 1Hz

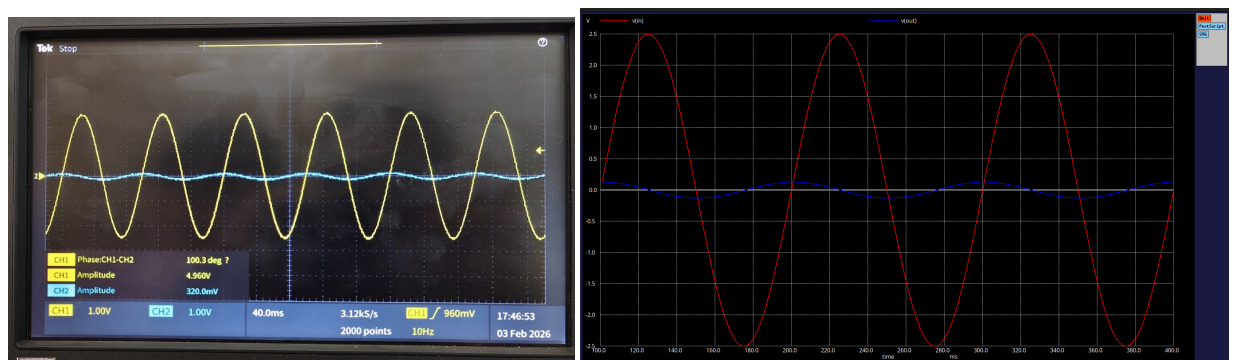


Figure 25: High pass filter with frequency 10Hz

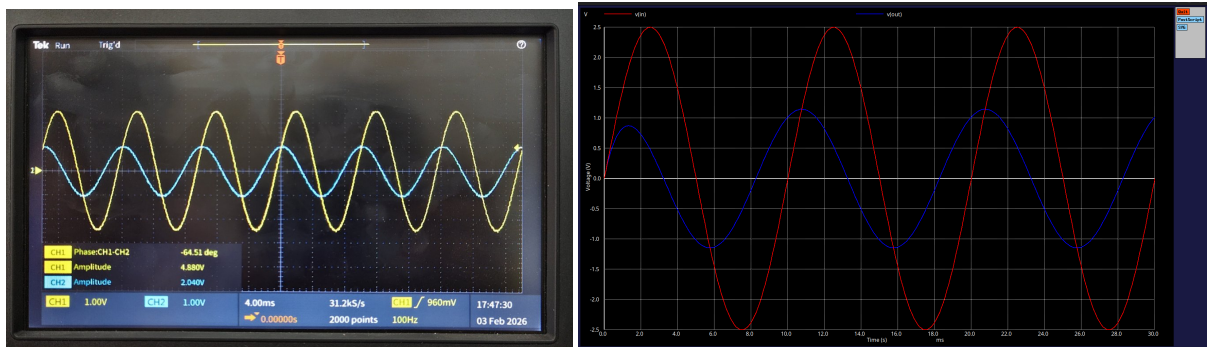


Figure 26: High pass filter with frequency 100Hz

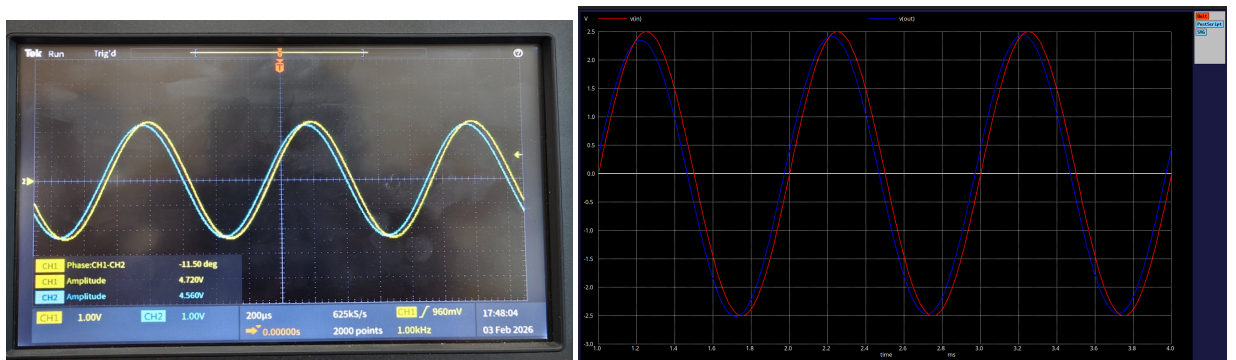


Figure 27: High pass filter with frequency 1kHz

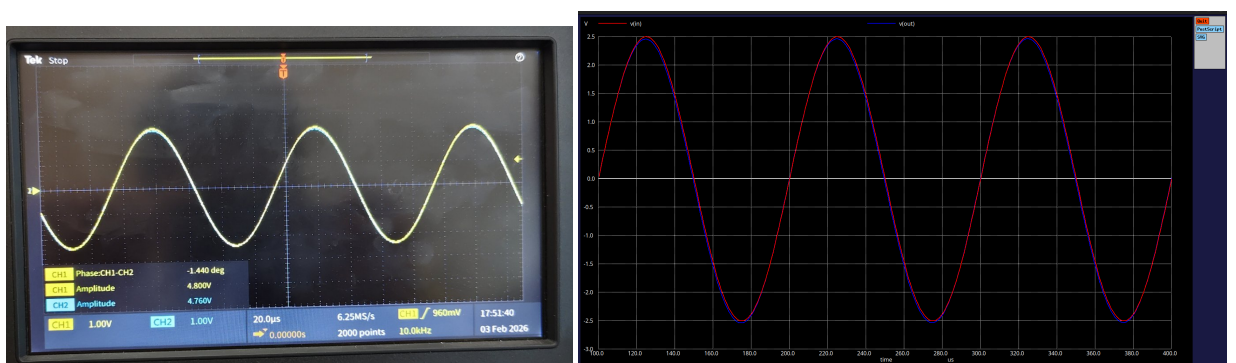


Figure 28: High pass filter with frequency 10kHz

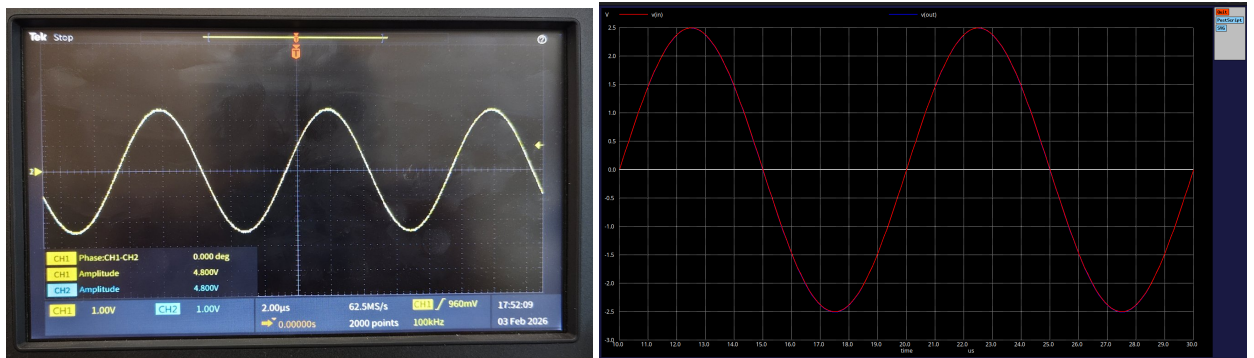


Figure 29: High pass filter with frequency 100kHz

5.4 Graphs:

Magnitude Response

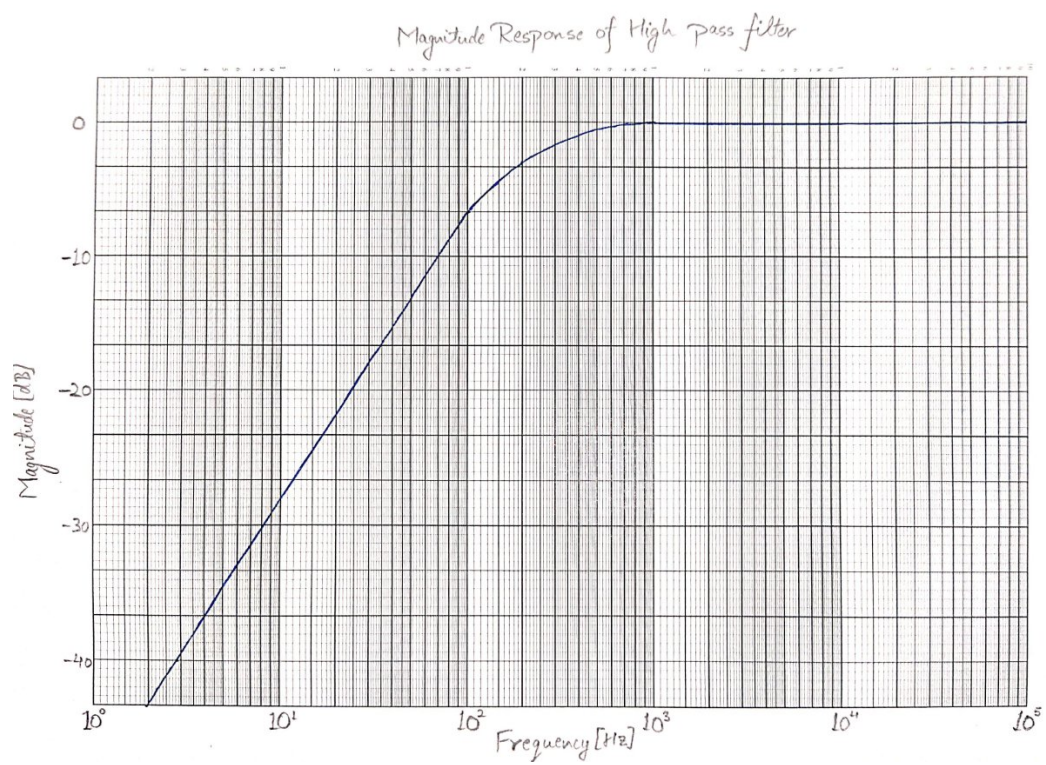


Figure 30: Experimental Plot of a High pass filter

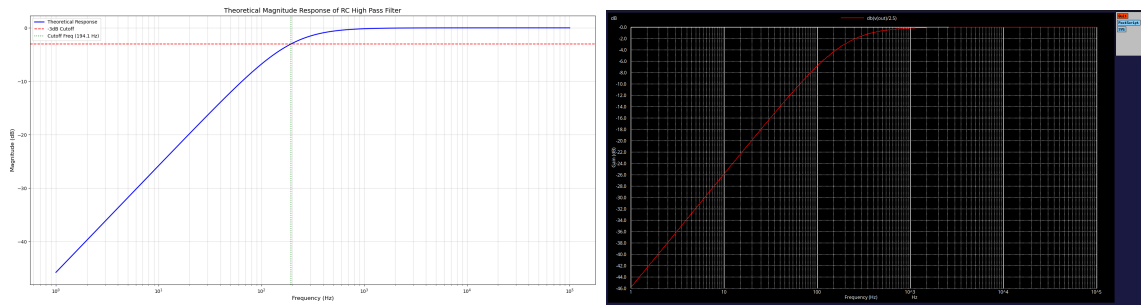


Figure 31: Python plot and ngspice plot of a High pass filter

Phase Response

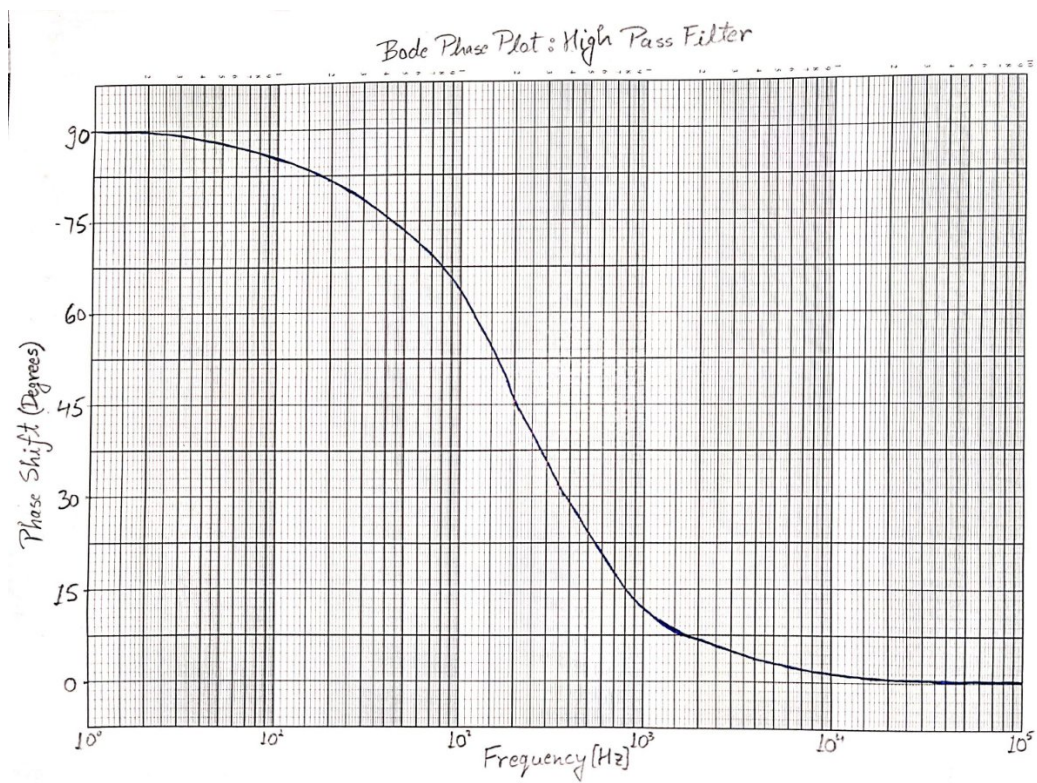


Figure 32: Experimental Plot of a High pass filter

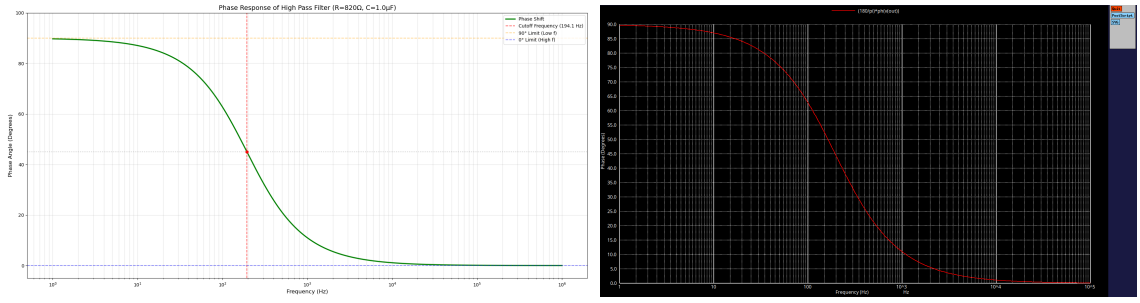


Figure 33: Python plot and ngspice plot of a High pass filter for phase response

Above Experimental graph of phase response of High pass filter matches exactly with the python plot and ngspice plot

Cut-off frequency:

Cut-off frequency for the given circuit ($R = 820\Omega$ and $C = 1\mu\text{F}$) given by

$$f_c = \frac{1}{2\pi RC} \quad (65)$$

$$\Rightarrow f_c = \frac{1}{2\pi \times 820 \times 10^3 \times 1 \times 10^{-6}} \quad (66)$$

$$\Rightarrow f_c = 194.09\text{Hz} \quad (67)$$

Slope:

- $\omega < \omega_c$, the slope is a constant +20 dB/decade. Means the signal is attenuated at lower frequencies.
- $\omega = \omega_c$ This is the point of the curve where the slope begins to transition.
- $\omega > \omega_c$, the slope is approximately 0 dB/decade. Means the signal passes through with almost no loss in amplitude.

Frequency (Hz)	Linear Gain $ H(f) $	Output Voltage V_{out} (V)	Gain (dB)
1	0.0051	0.0257	-45.7600
10	0.0514	0.2573	-25.7700
100	0.4579	2.2895	-6.7840
10^3	0.9816	4.9084	-0.1610
10^4	0.9998	4.9990	-0.0010
10^5	1.0000	5.0000	0.0000

Table 2: Gain at different frequencies ($R = 820\Omega$, $C = 1\mu\text{F}$, $V_{in} = 5\text{V}$)